

---

# 16-BIT ARITHMETIC LOGIC UNIT (ALU)

---

Name	SEC	ID
Ahmed Hassan Abdelhalim Labib	1	91240075
Mohamed Diaa Eldin	3	91240665

**Supervised by and presented to Eng. Ahmed Atef**

# Contents

<b>1. Overview.....</b>	<b>3</b>
<b>2. Architecture Specifications .....</b>	<b>3</b>
<b>3. Functional Blocks.....</b>	<b>3</b>
<b>4.     Status Flag .....</b>	<b>3</b>
<b>5.     Code .....</b>	<b>5</b>
<b>6.     Testbench .....</b>	<b>8</b>
<b>7.     Simulation .....</b>	<b>10</b>
<b>8.     GitHub .....</b>	<b>12</b>

## 1. Overview

This module implements a 16-bit Arithmetic Logic Unit (ALU) designed for a custom processor architecture. It performs arithmetic, bitwise logical, and shift operations based on a 5-bit control signal ( $F$ ). The design features a comprehensive Status Register to support conditional branching and complex arithmetic (both signed and unsigned).

## 2. Architecture Specifications

- **Data Width:** 16-bit signed/unsigned integers.
- **Control Width:** 5-bit Opcode ( $F$ ), allowing for up to 32 distinct operations.
- **Input Stage:** Two 16-bit operands ( $A$ ,  $B$ ) and a 1-bit Carry Input ( $C_{in}$ ).
- **Output Stage:** One 16-bit `Result` and a 6-bit `Status Vector`.
- **Design Type:** Purely combinational logic (`always @(*)`), ensuring result validity immediately after propagation delay.

## 3. Functional Blocks

The ALU is divided into three primary logical groups:

1. **Arithmetic Unit ( $F = 00000 - 00111$ ):**
  - Supports Addition (`ADD`) and Subtraction (`SUB`).
  - Supports operations with Carry/Borrow (`ADC`, `SBB`) for multi-word arithmetic.
  - Includes Increment (`INC`) and Decrement (`DEC`).
  - *Note:* Flags (Overflow, Aux Carry) are calculated manually to ensure precision for signed arithmetic.
2. **Logic Unit ( $F = 01000 - 01011$ ):**
  - Standard bitwise operations: `AND`, `OR`, `XOR`, and `NOT` (1's complement).
3. **Shift/Rotate Unit ( $F = 10000 - 10111$ ):**
  - Performs Logical Shifts (Left/Right).
  - Performs Rotations involving the Carry flag (Rotate through Carry), allowing for efficient bit-stream manipulation.

## 4. Status Flag

### 1. Carry Flag (C) – Bit [5]

- **Function:** Indicates an arithmetic carry or borrow generated out of the Most Significant Bit (MSB).

- **Derivation:** The arithmetic operations are performed using a 17-bit width internally. The 17th bit (index 16) is extracted to determine the Carry flag.
- **Formula:**  $C = \text{Result}[16]$

## 2. Zero Flag (Z) – Bit [4]

- **Function:** Indicates whether the output of the operation is effectively zero.
- **Derivation:** This is calculated using a logical NOR reduction across all 16 bits of the result. If any single bit in the result is high (1), the Zero flag is cleared to 0.
- **Formula:**  $Z = (\text{Result} == 0)$

## 3. Negative Flag (N) – Bit [3]

- **Function:** Indicates if the result is negative when interpreted as a signed Two's Complement number.
- **Derivation:** In Two's Complement notation, the MSB determines the sign. The ALU simply copies the MSB of the result to this flag.
- **Formula:**  $N = \text{Result}[15]$

## 4. Overflow Flag (V or OF) – Bit [2]

- **Function:** Indicates Signed Overflow. This occurs when the result of an arithmetic operation exceeds the capacity of the 16-bit signed range (-32,768 to +32,767).
- **Derivation:** Overflow logic detects cases where the result sign is mathematically impossible given the operand signs:
- **Addition:** Overflow occurs if adding two positive numbers yields a negative result, or adding two negative numbers yields a positive result.
- **Subtraction:** Overflow occurs if subtracting a negative number from a positive number yields a negative result (and vice versa).
- **Formula (Addition):**  $OF = (A[15] == B[15]) \ \&\& \ (\text{Result}[15] != A[15]);$

## 5. Parity Flag (P) – Bit [1]

- **Function:** Indicates the parity of the result. This design implements Even Parity, meaning the flag is set high if the result contains an even number of 1s.
- **Derivation:** This is calculated using an XNOR reduction of all bits in the result.
- **Formula:**  $P = \text{XNOR}(\text{Result}[15:0])$

## 6. Auxiliary Carry Flag (AC or Aux) – Bit [0]

- **Function:** Indicates a carry-out or borrow-out specifically from the lower nibble (Bit 3).

- **Derivation:** The ALU monitors the summation of the first 4 bits (3:0). If the sum exceeds 15 (0xF), the Aux flag is asserted.
- **Formula:**  $AUX = (A[3:0] + B[3:0] + C\_in) > 15$

## 5. Code

```

1 module alu (
2     input  [15:0] A,
3     input  [15:0] B,
4     input  [4:0]  F,
5     input                Cin,
6     output reg [15:0] Result,
7     output [5:0]  Status // {C, Z, N, V, P, A}
8 );
9
10    reg      C;
11    reg      V;
12    reg      Aux;
13
14
15    assign Status[5] = C;
16    assign Status[4] = (Result == 16'h0000);
17    assign Status[3] = Result[15];
18    assign Status[2] = V;
19    assign Status[1] = ~^Result;
20    assign Status[0] = Aux;
21
22    always @(*) begin
23
24        Result  = 16'h0000;
25        C      = 0;
26        V      = 0;
27        Aux    = 0;
28
29        case (F)
30
31 /*=====Arithmetic=====*/
32            5'b00000: begin
33                Result = 16'h0000;
34                C=0;
35                V=0;
36                Aux=0;
37            end
38
39            5'b00001: begin
40                {C,Result} = A + 1'b1;
41                V  = (A == 16'h7FFF);
42                Aux = (({1'b0, A[3:0]} + 1'b1) > 5'hF);
43            end

```

```

44
45      5'b00010: begin
46          Result = 16'h0000;
47          C=0;
48          V=0;
49          Aux=0;
50      end
51
52      5'b00011: begin
53          {C,Result} = A - 1'b1;
54          // C    = ~Res[16];
55          V    = (A == 16'h8000);
56          Aux   = (A[3:0] == 4'h0);
57      end
58
59      5'b00100: begin
60          {C,Result} = A + B;
61          V    = (A[15] == B[15]) && (Result[15] != A[15]);
62          Aux = ((1'b0, A[3:0]) + (1'b0, B[3:0])) > 5'hF;
63      end
64
65      5'b00101: begin
66          {C,Result} = A + B + Cin;
67          V    = (A[15] == B[15]) && (Result[15] != A[15]);
68          Aux = ((1'b0, A[3:0]) + (1'b0, B[3:0]) + Cin) > 5'hF;
69      end
70
71      5'b00110: begin
72          {C,Result} = A - B;
73          V    = (A[15] != B[15]) && (Result[15] != A[15]);
74          Aux   = (A[3:0] < B[3:0]);
75      end
76
77      5'b00111: begin
78          {C,Result} = A - B - Cin;
79          V    = (A[15] != B[15]) && (Result[15] != A[15]);
80          Aux   = ((1'b0, A[3:0]) < ((1'b0, B[3:0]) + Cin));
81      end
82
83
84 /*=====logic=====*/
85
86
87      5'b01000: Result = A & B;
88      5'b01001: Result = A | B;
89      5'b01010: Result = A ^ B;
90      5'b01011: Result = ~A;
91
92
93
94 /*=====Shift=====*/
95

```

```

96         5'b10000: begin
97             C = A[15];
98             Result = A << 1;
99         end
100
101         5'b10001: begin
102             C = A[0];
103             Result = A >> 1;
104         end
105
106         5'b10010: begin
107             C = A[15];
108             Result = A << 1;
109         end
110
111         5'b10011: begin
112             C = A[0];
113             Result = {A[15], A[15:1]};
114         end
115
116         5'b10100: begin
117             C = A[15];
118             Result = {A[14:0], A[15]};
119         end
120
121         5'b10101: begin
122             C = A[0];
123             Result = {A[0], A[15:1]};
124         end
125
126         5'b10110: begin
127             C = A[15];
128             Result = {A[14:0], Cin};
129         end
130
131         5'b10111: begin
132             C = A[0];
133             Result = {Cin, A[15:1]};
134         end
135
136         default: begin
137             Result = 16'h0000;
138             C=0;
139             V=0;
140             Aux=0;
141         end
142     endcase
end
endmodule

```

## 6. Testbench

```
1 `timescale 1ns / 1ps
2
3 module alu_tb;
4     reg [15:0] A;
5     reg [15:0] B;
6     reg [4:0] F;
7     reg      Cin;
8     wire [15:0] Result;
9     wire [5:0] Status; // Status Flags [C, Z, N, V, P, A]
10    wire C_flag = Status[5];
11    wire Z_flag = Status[4];
12    wire N_flag = Status[3];
13    wire O_flag = Status[2];
14    wire P_flag = Status[1];
15    wire A_flag = Status[0];
16    alu uut (
17        .A(A),
18        .B(B),
19        .F(F),
20        .Cin(Cin),
21        .Result(Result),
22        .Status(Status)
23    );
24
25    initial begin
26        A = 0;
27        B = 0;
28        F = 0;
29        Cin = 0;
30
31    /*=====Arithmetic=====*/
32        // 1. F = 00000: N/A
33        F = 5'b00000; A = 16'h0000; B = 16'h0000; Cin = 0;
34        #10;
35        // 2. F = 00001: INC (Increment A)
36        F = 5'b00001; A = 16'h0B05; B = 16'h0000; Cin = 0;
37        #10;
38        // 3. F = 00010: N/A
39        F = 5'b00010; A = 16'h0B05; B = 16'h0000; Cin = 0;
40        #10;
41        // 4. F = 00011: DEC (Decrement A)
42        F = 5'b00011; A = 16'h0B05; B = 16'h0006; Cin = 0;
43        #10;
44        // 5. F = 00100: ADD
```



```

45     F = 5'b00100; A = 16'h0BA5; B = 16'h0003; Cin = 0;
46     #10;
47     // ADD Overflow Test
48     F = 5'b00100; A = 16'h7FFF; B = 16'h0001; Cin = 0;
49     #10;
50     // 6. F = 00101: ADD CARRY
51     F = 5'b00101; A = 16'h0AB5; B = 16'h0CF3; Cin = 1;
52     #10;
53     // 7. F = 00110: SUB
54     F = 5'b00110; A = 16'h050A; B = 16'h0BAC; Cin = 0;
55     #10;
56     // 8. F = 00111: SUB BORROW
57     F = 5'b00111; A = 16'h000A; B = 16'h0003; Cin = 1;
58     /*=====logic=====*/
59     #10;
60     // 9. F = 01000: AND
61     F = 5'b01000; A = 16'hFFFF; B = 16'h00FF; Cin = 0;
62     #10;
63     // 10. F = 01001: OR
64     F = 5'b01001; A = 16'hF000; B = 16'h000F; Cin = 0;
65     #10;
66     // 11. F = 01010: XOR
67     F = 5'b01010; A = 16'hAAAA; B = 16'h5555; Cin = 0;
68     #10;
69     // 12. F = 01011: NOT
70     F = 5'b01011; A = 16'h1010; B = 16'h0000; Cin = 0;
71     /*=====Shift=====*/
72     #10;
73     // 13. F = 10000: SHL (Shift Left Logical)
74     F = 5'b10000; A = 16'h0501; B = 16'h0001; Cin = 0;
75     #10;
76     // 14. F = 10001: SHR (Shift Right Logical)
77     F = 5'b10001; A = 16'h0C02; B = 16'h0001; Cin = 0;
78     #10;
79     // 15. F = 10010: SAL (Arithmetic Shift Left)
80     F = 5'b10010; A = 16'h7FFF; B = 16'h0001; Cin = 0;
81     #10;
82     // 16. F = 10011: SAR (Arithmetic Shift Right)
83     F = 5'b10011; A = 16'h80F0; B = 16'h0001; Cin = 0;
84     #10;
85     // 17. F = 10100: ROL (Rotate Left)
86     F = 5'b10100; A = 16'h8001; B = 16'h0001; Cin = 0;
87     #10;
88     // 18. F = 10101: ROR (Rotate Right)
89     F = 5'b10101; A = 16'h8001; B = 16'h0001; Cin = 0;
90     #10;
91     // 19. F = 10110: RCL (Rotate Through Carry Left)
92     F = 5'b10110; A = 16'h8008; B = 16'h0001; Cin = 1;
93     #10;
94     // 20. F = 10111: RCR (Rotate Through Carry Right)
95     F = 5'b10111; A = 16'h8009; B = 16'h0001; Cin = 1;
96     #10;


```



```


97      /*=====Sheet Cases=====*/
98      F = 5'b00111; A = 16'h0085; B = 16'h0095; Cin = 1;
99      #10;          // CASE 1: SBB AL, BL (AL=85, BL=95, CF=1)
100     F = 5'b00100; A = 16'h0089; B = 16'h0087; Cin = 0;
101     #10;          // CASE 2: ADD AL, 87 (AL=89)
102     F = 5'b10101; A = 16'h0082; B = 16'h000A; Cin = 0;
103     #10;          // CASE 3: ROR AL, CL (AL=82, CL=0A)
104     F = 5'b10010; A = 16'h0073; B = 16'h0001; Cin = 0;
105     #10;          // CASE 4: SAL AL, 1 (AL=73)
106     F = 5'b10111; A = 16'h0073; B = 16'h0001; Cin = 1;
107     #10;          // CASE 5: RCR AL, 1 (AL=73, CF=1)
108     F = 5'b00100; A = 16'h0006; B = 16'h0005; Cin = 0;
109     #10;          // CASE 6: ADD BL, 05 (BL=06)
110     F = 5'b01010; A = 16'h0055; B = 16'h00FF; Cin = 0;
111     #10;          // CASE 7: XOR AL, FF (AL=55)
112     F = 5'b00110; A = 16'h56BC; B = 16'h47CD; Cin = 0;
113     #10;          // CASE 8: SUB AX, BX (AX=56BC, BX=47CD)
114     F = 5'b00100; A = 16'h7FFF; B = 16'h3333; Cin = 0;
115     #10;          // CASE 9: ADD DX, CX (DX=7FFF, CX=3333)
116     F = 5'b01000; A = 16'h5555; B = 16'h5AAA; Cin = 0;
117     #10;          // CASE 10: AND AX, BX (AX=5555, CX/BX=5AAA)
118     $stop;
119 end
120
121 endmodule

```

## 7. Simulation

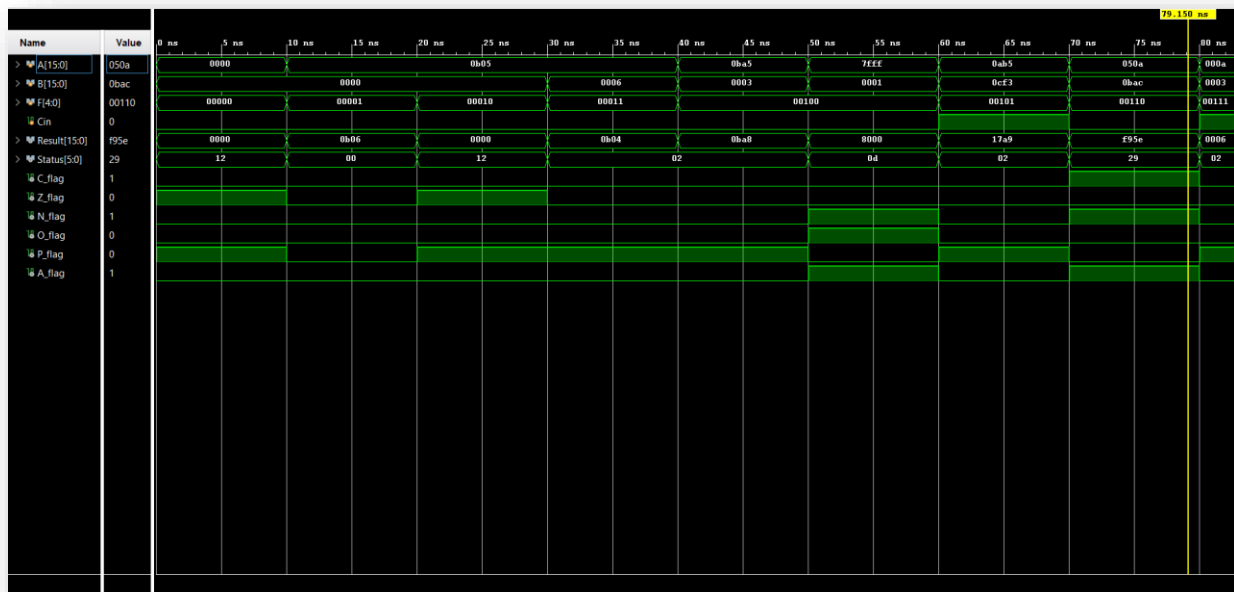

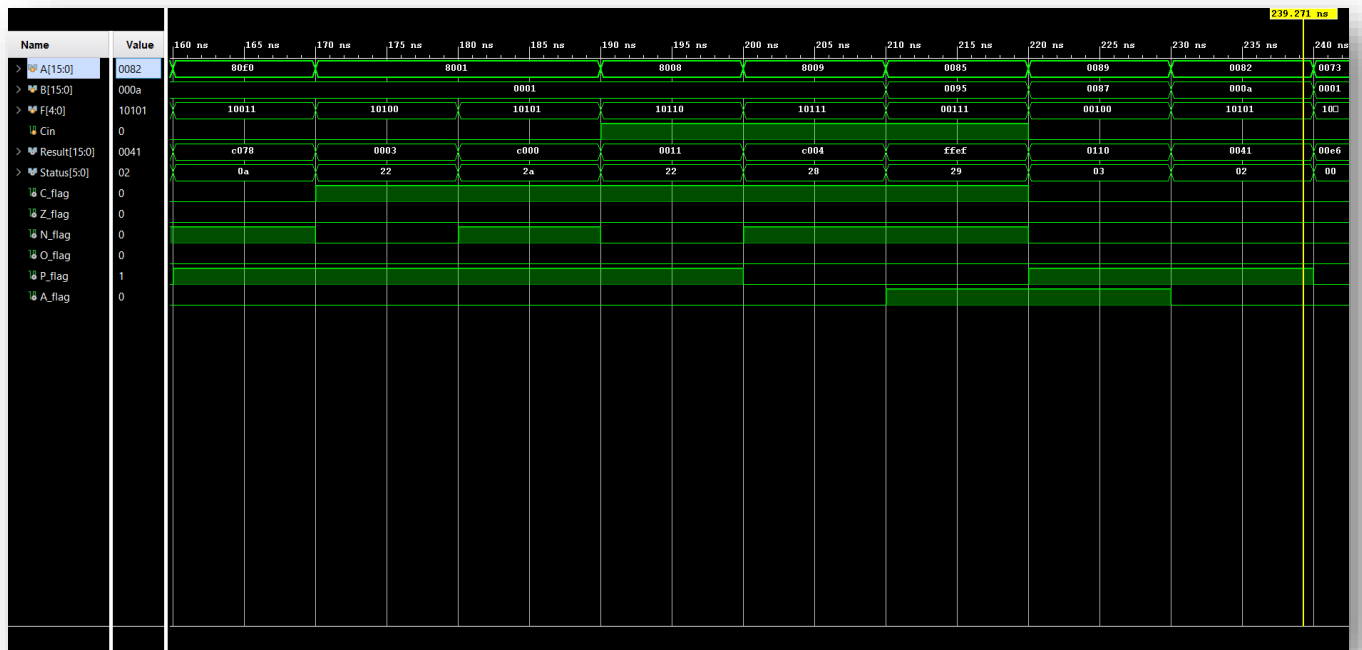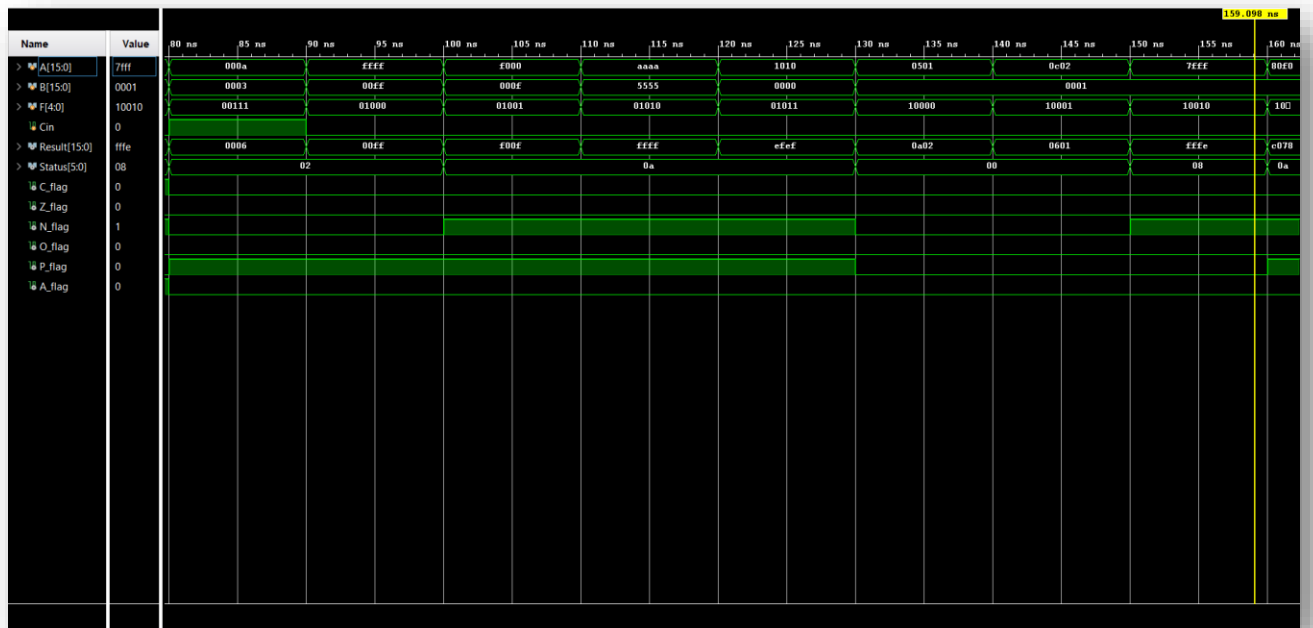

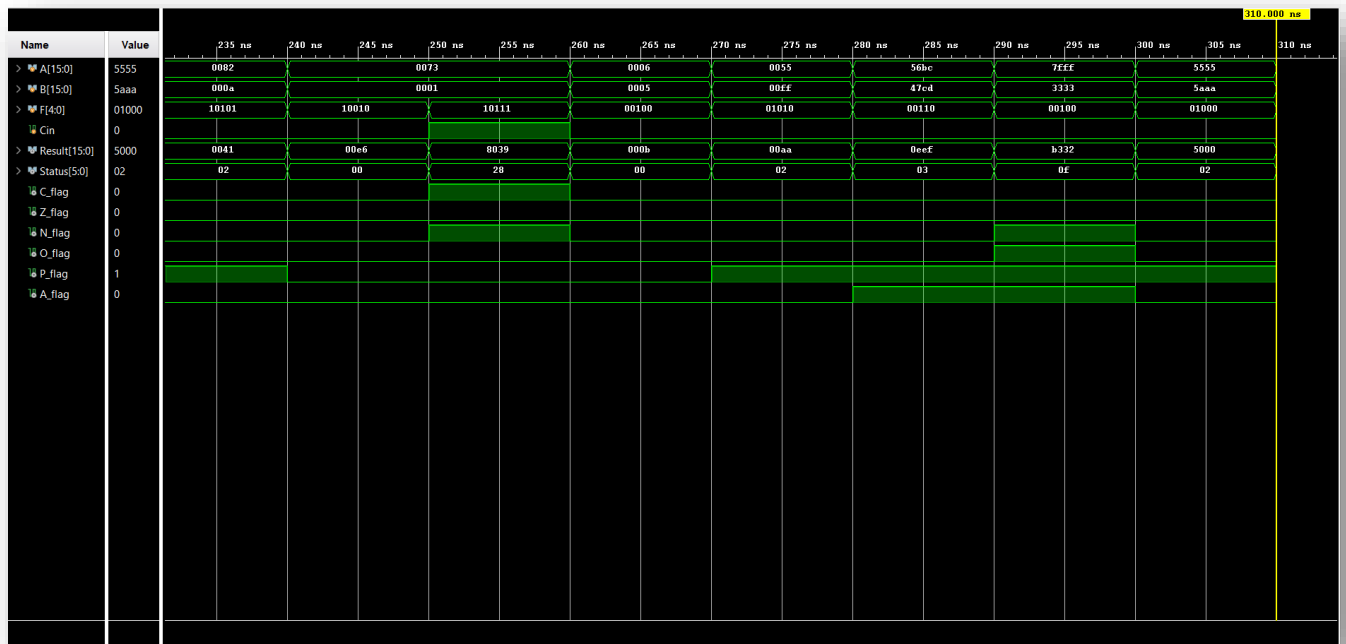

## 8. GitHub

Link: <https://github.com/a7med57/16-Bit-ALU-.git>